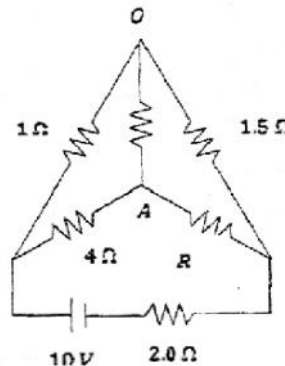


**I/IV B. Tech. DEGREE EXAMINATIONS, DECEMBER - 2016****Second Semester****BT / CSE / ECE / EEE****BASIC ELECTRICAL AND ELECTRONIC SCIENCES**Time : **Three Hours**Maximum Marks : **60****Answer Question No. 1 Compulsory.****12x1=12 M****Answer ONE question from each Unit.****4x12=48 M**

1. a) Define active and passive elements ?
- b) Define charge and current ?
- c) What is power factor ?
- d) Define alternative current and give an example ?
- e) Define faraday's law ?
- f) What are the applications of Zener diode ?
- g) What are the advantages of DVMs ?
- h) Define indicating type instrument.
- i) Write expression for mutual inductance ?
- j) What is break down voltage ?
- k) Which configuration of transistor is used for current amplification ?
- l) What are the applications of FET ?

**UNIT - I**

2. a) Define (i) Peak value (ii) Average value (iii) Peak factor (iv) Form factor and write its values to sine wave.
- b) Find the value of R and the current flowing through it in the circuit shown when the current in branch OA is zero. Workout the problem stating the reasons at different steps.

**P.T.O.**

(OR)

3. a) State and explain kirchoff's laws applied to electrical circuits ?
- b) Explain power triangles and impedance triangles with examples.

**UNIT - II**

4. a) Derive the expression for co-efficient of coupling a coupled inductor ?
- b) Classify different types of measuring instruments ?

(OR)

5. a) State the principles on induction and distinguish static and dynamically induced emfs ?
- b) Explain the principle of operation of DVM ?

**UNIT - III**

6. a) Draw and explain the characteristics of Zener diode ?
- b) Explain the working of full wave rectifier with L load ?

(OR)

7. a) Explain the working of SCR and write its applications ?
- b) Compare the characteristics of UJT and transistor ?

**UNIT - IV**

8. a) Explain the operation of BJT and discuss the current due to electrons and holes in PNP transistor ?
- b) Discuss the operation of MOSFET with a neat sketch ? Derive expression for  $R_{ON}$  ?

(OR)

9. a) Explain the operation SCR using two transistor model ?
- b) Write a note on common base configuration of transistor ?



**I/IV B. Tech. DEGREE EXAMINATIONS, APRIL / MAY - 2016**  
**SECOND SEMESTER**  
**BT / CSE / ECE / EEE**  
**BASIC ELECTRICAL AND ELECTRONIC SCIENCES**

---

---

Time : **Three Hours**Maximum Marks : **60****Answer Question No. 1 Compulsory.****12x1=12 M****Answer ONE question from each Unit.****4x12=48 M**

1. a) What is form factor ?
- b) What is reactive power ?
- c) Define rms value ?
- d) What is mutual inductance ?
- e) Define Faraday's law of electromagnetic induction ?
- f) Write different types of DVMs ?
- g) What are the dominant carriers in NPN transistor ?
- h) What is peak inverse voltage ?
- i) Write the applications of MOSFET ?
- j) Draw the output characteristics of CC configuration ?
- k) Write the applications of SCR ?
- l) What is the form factor of full wave rectifier ?


**UNIT - I**

2. a) State and explain kirchoff's laws and give an examples for each.
- b) When load is applied to  $10\Omega$  a unknown voltage source a current of 2.5A flows and when the load resistance is increased to  $20\Omega$ , the current drops to 2A. If a load of  $15\Omega$  is connected across the source, what is the voltage across is it ? Also calculate the power dissipated in the circuit.

(OR)

3. a) Draw and explain vector diagrams for series RL, RC circuits ?

- b) Calculate the power delivered to  $16\Omega$  in the circuit shown in Fig.

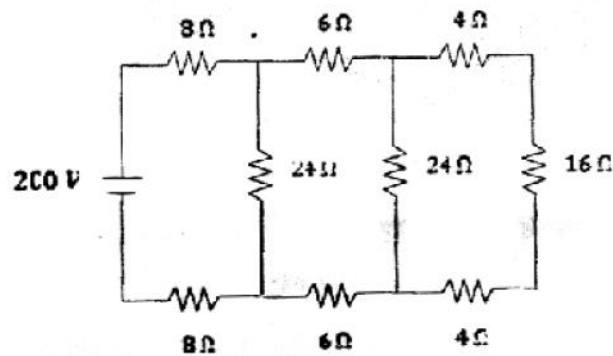**UNIT - II**

4. a) Derive the expression for dynamically induced emf ?  
 b) Write the principle and operation of CRO ?
- (OR)
5. a) Derive the expression for energy stored in magnetic fields ?  
 b) Two coupled coils have self inductances  $0.001\text{ H}$  and  $0.002\text{ H}$  respectively. The coefficient of coupling between two coils is  $0.75$ . Find voltage in the second coil and the flux of first coil provided the second coil has  $500$  turns and the circuit current is given by  $i_1 = 2 \sin 314t\text{ A}$ .

**UNIT - III**

6. a) With the help of neat sketch explain the working of diode ?  
 b) Explain the working of UJT and give its applications ?
- (OR)
7. a) Explain turn-on characteristics of SCR with a neat sketch ?  
 b) Draw and explain the working of Bridge rectifier with R load ?

**UNIT - IV**

8. a) Discuss the operation BJT and its characteristics ?  
 b) Explain the characteristics of JFET ?
- (OR)
9. a) Compare N-channel and P-channel MOSFET ?  
 b) Draw the input and output characteristics of common emitter configuration ?

